



## **Department of IT and Computer Science**

**Pak-Austria Fachhochschule: Institute of Applied Sciences and  
Technology, Haripur, Pakistan**

# **COMP-261L Computer Organization and Assembly Language**

## **Final Project Report Group 1**

**Muhammad Suleman  
B20F0012CS035**

**Yaseen Ejaz Ahmed  
B20F0283CS014**

**Muhammad Danish  
B20F0375CS030**

**Submitted to: Dr. Hashim Ali**

---

**Instructor Signature**

# Table of Contents

<b>Section 1: Introduction</b>	3
Section 1.1: Objective	3
<b>Section 2: Problem Statement</b>	3
<b>Section 3: Components</b>	4
Section 3.1: Register File	4
Section 3.2: Data Memory	4
Section 3.3: Instruction Memory	5
Section 3.4: Program Counter	5
Section 3.5: ALU (4 Bit)	5
<b>Section 4: Controller</b>	6
Section 4.1: Truth Table	6
Section 4.2: K-Map Simplification	6
Section 4.2.1: A1	6
Section 4.2.2: A0	6
Section 4.2.3: A/S	7
Section 4.2.4: Cin	7
Section 4.2.5: RWR	7
Section 4.2.6: MRD	8
Section 4.2.7: MWR	8
Section 4.2.8: RegD	8
Section 4.2.9: MemToReg	9
Section 4.2.10: ALUSRC	9
Section 4.2.11: BR	9
Section 4.2.12: J	9
Section 4.3: Circuit	10
<b>Section 5: Final Microprocessor</b>	11
<b>Section 6: Testing</b>	12
<b>Section 7: Step by Step</b>	16
<b>Section 8: Conversion to HEX</b>	18
<b>Section 9: Conclusion</b>	18

# Microprocessor Design

## Section 1: Introduction

This document is a project report for a simple MIPS microprocessor architecture. The project's purpose is to develop a 4-bit processor at the logic level, then replicate it at the layout level. With a custom-defined instruction set, this document explains the fundamental concepts of microprocessor design in the simplest way possible. Logisim was used to create the project.

### Section 1.1: Objective:

The purpose of this project is to recreate all the basic building elements of a RISC-based microprocessor so that a complete data-path and control unit can be designed. Later, in order to test the processor's operation, a basic program must be written to test the operation of components as well as the microprocessor itself.

## Section 2: Problem Statement

Build a Processor using all the concepts that you have learnt in this course. The processor must have all the necessary components required to run a simple C code. The code that you must run and test on your microprocessor is as follows:


$$A \leftarrow 0$$
$$B \leftarrow 0$$
$$C \leftarrow 0$$
$$A \leftarrow A + 7$$
$$B \leftarrow B - 8$$
$$C \leftarrow \text{DMEM}[2] \leftarrow 0$$
$$\text{IF } (C) \text{ THEN } C \leftarrow A + B \text{ ELSE } \{B \leftarrow B \mid 7; A \leftarrow B \& 7;\}$$
$$C \leftarrow A + B$$
$$\text{DMEM}[15] \leftarrow C$$

## Section 3: Components

Following are the components we need to make our Microprocessor.

 
### Section 3.1: Register File

Registers are used to temporarily store data for the microprocessor. This makes the microprocessor faster. It has 4 address lines to represent 4 bit data lines.



 
### Section 3.2: Data Memory

The Data Memory is used to permanently store data. It is slower to retrieve data from the data memory compared with the registers. Data is loaded from Data Memory to registers for faster processing. It consists of 4 address lines for 4 bit data lines.



 
### Section 3.3: Instruction Memory

The Instruction Memory holds all the instructions to be executed.



 
### Section 3.4: Program Counter

The Program Counter is used to retrieve the next instruction to be executed in the Instruction Memory. It is a 4 bit counter with 1 increment.


 
### Section 3.5: ALU (4 Bit)

The ALU is the main Arithmetic and Logic Unit. It can perform AND, OR, ADD, and SUB operations. It takes two inputs each of 4 bits and gives result in 4 bits. It has Flags for output.



## Section 4: Controller

### Section 4.1: Truth Table

Following is the Controller Input/Output table.

FUNC	Type	Input	Output										
		Op	A1A0	A/S	Cin	RWR	MRD	MWR	RegD(LW)	MtoRegSW	aluSrc	Br	J
AND	R	0000	00	x	x	0	1	1	1	0	0	0	0
OR	R	0001	01	x	x	0	1	1	1	0	0	0	0
ADD	R	0010	10	0	0	0	1	1	1	0	0	0	0
SUB	R	0011	10	1	1	0	1	1	1	0	0	0	0
ANDi	I	0100	00	x	x	0	1	1	0	0	1	0	0
ORi	I	0101	01	x	x	0	1	1	0	0	1	0	0
ADDi	I	0110	10	0	0	0	1	1	0	0	1	0	0
SUBi	I	0111	10	1	1	0	1	1	0	0	1	0	0
SLT	R	1000	11	1	1	0	1	1	1	0	0	0	0
SLTi	I	1001	11	1	1	0	1	1	0	0	1	0	0
BEQ	I	1010	10	1	1	1	x	x	x	x	0	1	0
BNE	I	1011	10	1	1	1	x	x	x	x	0	1	0
J	J	1100	xx	x	x	x	x	x	x	x	x	0	1
Unuse	---	1101	xx	x	x	x	x	x	x	x	x	x	x
LW	I	1110	10	0	0	0	0	1	0	1	1	0	0
SW	I	1111	10	0	0	1	1	0	x	0	1	0	0

Note: RWR, MRD, and MWR are active low.

### Section 4.2: K-Map Simplification

#### Section 4.2.1: A1

AB/CD	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	x	x	1	1
10	1	1	1	1

Simplified Equation:  $A + C$

#### Section 4.2.2: A0

AB/CD	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	x	x	0	0
10	1	1	0	0

Simplified Equation:  $C'D + AC'$

**Section 4.2.3: A/S**

AB/CD	00	01	11	10
00	x	x	1	0
01	x	x	1	0
11	x	x	0	0
10	1	1	1	1

Simplified Equation:  $AC' + A'D$

**Section 4.2.4: Cin**

AB/CD	00	01	11	10
00	x	x	1	0
01	x	x	1	0
11	x	x	0	0
10	1	1	1	1

Simplified Equation:  $AC' + A'D$

**Section 4.2.5: RWR**

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	x	x	1	0
10	0	0	1	1

$AB'C + ACD$

Simplified Equation:  $AC(B'+D)$

**Section 4.2.6: MRD**

AB/CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	x	x	1	0
10	1	1	x	x

Simplified Equation:  $A' + B' + D$

**Section 4.2.7: MWR**

AB/CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	x	x	0	1
10	1	1	x	x

$A' + B' + D'$

Simplified Equation:  $(ABD)'$

**Section 4.2.8: RegD**

AB/CD	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	x	x	x	0
10	1	0	x	x

$A'B' + B'C'D'$

Simplified Equation:  $B'(A' + C'D')$



**Section 4.2.9: MemToReg**

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	x	x	0	1
10	0	0	x	x

Simplified Equation:  $ABD'$ **Section 4.2.10: ALUSRC**

AB/CD	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	x	x	1	1
10	0	1	0	0

Simplified Equation:  $B + AC'D$ **Section 4.2.11: BR**

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	x	0	0
10	0	0	1	1


Simplified Equation:  $AB'CD$ **Section 4.2.12: J**

AB/CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	x	0	0
10	0	0	0	0

Simplified Equation:  $ABC'$
 
### Section 4.3: Circuit

The controller chip shall take four inputs and decodes them to outputs for the control signals. This has been constructed after simplification.





## Section 6: Testing

Now, we will test the microprocessor that we designed, using the code provided in the problem statement.

R0=A, R1=B, R2=C, R3=D

**PC = 0x0000**

ADDi R0,R0,7

0000 0110 00 00 0111

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Immediate
0000	0110	00	00	0111

R<sub>s</sub> = R0

R<sub>t</sub> = R0

Immediate = 0x0111 or (7)<sub>10</sub>

**PC = 0x0001**

SUBi R1,R1,8

0000 0111 01 01 1000

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Immediate
0000	0111	01	01	1000

R<sub>s</sub> = R1

R<sub>t</sub> = R1

Immediate = 0x1000 or (8)<sub>10</sub>

**PC = 0x0002**

LW R2, 2(R3)

0000 1110 11 10 0010

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Offset
0000	1110	11	10	0010

R<sub>s</sub> = R3R<sub>t</sub> = R2Offset = 0x0010 or (2)<sub>10</sub>**PC = 0x0003**

BNE R2, R3, 3

0000 1011 10 11 0111

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Address
0000	1011	10	11	0011

R<sub>s</sub> = R2R<sub>t</sub> = R3Address = 0x0011 or (3)<sub>10</sub>**PC = 0x0004**

ORi R1, R1, 7

0000 0101 01 01 0111

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Immediate
0000	0101	01	01	0111

R<sub>s</sub> = R2R<sub>t</sub> = R3Immediate = 0x0111 or (7)<sub>10</sub>

**PC = 0x0005**

ANDi R0, R1, 7

0000 0100 01 00 0111

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Immediate
0000	0100	01	00	0111

R<sub>s</sub> = R1R<sub>t</sub> = R0Immediate = 0x0111 or (7)<sub>10</sub>**PC = 0x0006**

J 0x1000

0000 1100 00 00 1000

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Address
0000	1100	xx	xx	1000

Address = 0x1000 or (8)<sub>10</sub>**PC = 0x0007**

ADD R2, R0, R1

0000 0010 00 01 10 00

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	R <sub>d</sub>	Unused
0000	0010	00	01	10	00

R<sub>s</sub> = R0R<sub>t</sub> = R1R<sub>d</sub> = R2

**PC = 0x0008**

ADD R2, R0, R1

0000 0010 00 01 10 00

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	R <sub>d</sub>	Unused
0000	0010	00	01	10	00

R<sub>s</sub> = R0R<sub>t</sub> = R1R<sub>d</sub> = R2**PC = 0x0009**

SW R2, 15(R3)

0000 1111 11 10 1111

Unused	Opcode	R <sub>s</sub>	R <sub>t</sub>	Offset
0000	1100	11	10	1111

R<sub>s</sub> = R3R<sub>t</sub> = R2Offset = 0x1111 or (15)<sub>10</sub>

## Section 7: Step by Step

### ADDi R0, R0, 7:

$$R0 = 0000 + 0111 = 0111$$

### SUBi R1, R1, 8

$$R1 = 0000 - 1000 = -(1000) = 1000$$

### LW R2, 2(R3)

$$R2 = 2 + 0x0000 = 0x0002$$

Value in 0x0002 is 0000

$$R2 = 0000$$

### BNE R2, R3, 0011

$$R2 = R3 = 0000$$

If ( $R2 \neq R3$ )

Branch

Else go to next instructions



**ORi R1, R1, 7**

$R1 = 1000$

$R1 = 1000 \mid 0111 = 1111$

**ANDi R0, R1, 7**

$R1 = 1111$

$R0 = 1111 \ \& \ 0111 = 0111$

**J 0x1000**

Unconditional Jump

**ADD R2, R0, R1**

*Branch Value*

**ADD R2, R0, R1**

$R0 = 0111$

$R1 = 1111$

$R2 = 1111 + 0111 = 0110$

**SW R2, 15(R3)**

R2 = 0110

R3 = 0000

Store 0110 in 15<sup>th</sup> address of Data Memory

**Section 8: Conversion to HEX**

PC	Instruction	Binary	Hexadecimal	Execution
0000	ADDi R0, R0, 7	0000 0110 0000 0111	0x0607	R0 = 0111
0001	SUBi R1, R1, 8	0000 0111 0101 1000	0x0758	R1 = 1000
0010	LW R2, 2(R3)	0000 1110 1110 0010	0x0EE2	R2 = 0000
0011	BNE R2, R3, 0011	0000 1011 1011 0111	0x0BB3	
0100	ORi R1, R1, 7	0000 0101 0101 0111	0x0557	R1 = 1111
0101	ANDi R0, R1, 7	0000 0100 0100 0111	0x0447	R0 = 0111
0110	J 1000	0000 1100 0000 1000	0x0C08	
0111	ADD R2, R0, R1	0000 0010 0001 1000	0x0218	R2 = 0110
1000	ADD R2, R0, R1	0000 0010 0001 1000	0x0218	R2 = 0110
1001	SW R2, 15(R3)	0000 1111 1110 1111	0x0FEF	DMEM[15] = 0110

**Section 9: Conclusion**

This project consists of the construction of a MIPS architecture microprocessor. The processor can perform operations like ADD, ADDi, SUB, SUBi, AND, ANDi, OR, ORi, LW, SW, J, BEQ, BNE. We can use codes to load in the Instruction Memory to perform the instructions. Many logics and operations have been applied to construct this microprocessor, and all the components like Program Counter, Instruction Memory, Register File, ALU, Data Memory, Multiplexers, and Controller were used and integrated together. Instead of going towards the shortcut of using a ROM as a controller, we went for the K-Map simplification approach to construct the controller of the processor as both methods can give accurate results. The project was run and tested by all the members of Group 1.

**THE END**